

# Analog Interview Questions

By

Ravi Dixit

[www.vlsiprojects.com](http://www.vlsiprojects.com)

[www.learnanalog.com](http://www.learnanalog.com)

Learn Analog

1. State whether True or False

- a) Electro migration depends on current.
- b) In LOCOS selective oxide growth is achieved using Silicon dioxide.
- c) CVD process does not consume underlying silicon

2. To remove antenna effect which method is used

(i) Metal Splitting (ii) Putting Antenna diode (iii) Metal Slotting (iv) Metal Over Etching

- (a) (i) and (iii) are true
- (b) (i) and (ii) are true
- (c) (i) (ii) and (iii) are true
- (d) (ii) and (iv) are true

3. In an Inverter circuit if the following condition lies for input voltage

$V_{in} = V_{dd}/2$  then

- (a) n-mos will be in cut off and p-mos will be in linear region
- (b) n-mos will be in linear and p-mos will be in cut off region
- (c) n-mos and p-mos both will be in cut off region
- (d) None of these

4) Calculate  $R_z$ ? ( Two NMOS are connected in diagram shown below )

 


Figure 1

- 5) If  $V_{g1}$  is fixed to 2.5V and  $V_{g2}$  is sweep from 0 to 5V, Draw  $V_{out}$  waveform ( assume  $V_{DD} = 5V$  )

 


Figure 2

- 6) Assume threshold voltage of PMOS is  $-V_t$  & NMOS is  $V_t$  , a input pulse from  $V_{SS}$  to  $V_{DD}$  is given to circuit shown below, Draw the output waveform



 
 


Figure 3

 

(Figure 4)

9) Tell me the advantages of amplifier shown in figure 5 over those shown in figure 4 ?

 

(Figure 5)

10) What is a miller compensation technique?

11) Draw an OPAMP & tell me various poles & zeros associated with the circuit you draw ? How you will stabilize your system?

- 14) What are main advantages of making CMOS circuits working in sub threshold regions?
- 15) Describe Electro migration effect? & ways to reduce Electro migration during layouts?
- 16) What is CMP dishing? How metal slotting & dummy metal help in reducing CMP dishing ?
- 17) Describe OPC techniques & phase shift mask?
- 18) What is Latch up? Tell me at least 5 ways how we can reduce probability of a latchup in ur circuit ?
- 19) Draw the layout of M1 & M2 transistor in figure 5 (hint : - take care of Matching pattern , Match routing & guard etc ) .
- 20 ) how you can match you resistor & capacitor layouts ?
- 21 ) what are advantages of Common centroid & interdigitized patterns

For more interview questions, please visit [www.vlsiprojects.com](http://www.vlsiprojects.com)